

KENDRIYA VIDYALAYA KORBA NO.4

CLASS -10

HOLIDAY HOMEWORK

1-WHAT IS RESISTOR?

2-DERIVE THE EQUIVALENT RESISTOR IN SERIES COMBINATION .

3-DERIVE THE EQUIVALENT RESISTOR IN PARALEEL COMBINATION.